

Digits Identifier Circuit for Euler's Number

PC/CP220 Revised Project Phase I

Himanya Verma
October 1st 2024

Description:

The project aims to design a circuit that identifies specific decimal digits of the mathematical constant e (approximately 2.71828) based on binary inputs representing decimal places (0-9). It will provide outputs corresponding to the binary representation of those digits.

Inputs:

The Digit Identifier Circuit will have four inputs:

1. **A0** (Least Significant Bit)
 - Input: 1 if included, 0 if not.
2. **A1**
 - Input: 1 if included, 0 if not.
3. **A2**
 - Input: 1 if included, 0 if not.
4. **A3** (Most Significant Bit)
 - Input: 1 if included, 0 if not.

Input Specification:

- The circuit will read the inputs as a 4-bit binary number (A3 A2 A1 A0), representing decimal places from 0 to 9.

Outputs:

The Digit Identifier Circuit will have at least ten outputs, each corresponding to a digit of e. The outputs will be:

1. **Digit 0** (O0)
2. **Digit 1** (O1)
3. **Digit 2** (O2)
4. **Digit 3** (O3)
5. **Digit 4** (O4)
6. **Digit 5** (O5)
7. **Digit 6** (O6)
8. **Digit 7** (O7)
9. **Digit 8** (O8)
10. **Digit 9** (O9)

Output Logic:

- An output will be set to '1' if it corresponds to the digit of e indicated by the binary input; otherwise, it will be set to '0'.
- The digits of e are:
 - 2.7182818284 → (0: 2, 1: 7, 2: 1, 3: 8, 4: 2, 5: 8, 6: 1, 7: 8, 8: 4, 9: 0)
- Example outputs:
 - Input 0000 (decimal 0) → Output 10 (binary for digit 2)
 - Input 0001 (decimal 1) → Output 111 (binary for digit 7)
 - Input 0010 (decimal 2) → Output 1 (binary for digit 1)
 - Input 0011 (decimal 3) → Output 1000 (binary for digit 8), etc.

Handling Combinations:

- For each binary input, only one output will be set to **1**, corresponding to the digit of e for the specified decimal place.
- If the input is outside the valid range (e.g., **1010** or greater), all outputs will be set to **0** as no valid digit exists for that input.

Error Conditions and Responses:

Invalid Input Range:

- Condition: When the binary input exceeds **0001 1001** (decimal 9), indicating an invalid request for digits beyond the 10th decimal place of ee.
- Response:
 - o Set all outputs (O0 to O9) to **0**..

Non-binary Inputs:

- Condition: If any input bit is not **0** or **1**.
- Response:
 - Set all outputs (O0 to O9) to **0**.

Ambiguous Possibilities:

Don't Care Conditions:

- Condition: There are no ambiguous possibilities in this design as each binary input uniquely corresponds to a single digit of e.
- Response:
 - If an input corresponds to a digit of e (within the range of 0-9), it will output the appropriate value.
 - If the input is outside the valid range or invalid (non-binary), all outputs will remain **0**, providing a clear indication of the error.

Multiple Outputs:

- Condition: Each input corresponds to exactly one output. There are no cases where multiple digits would activate simultaneously based on valid inputs.
- Response:
 - Ensure that for valid inputs, only the respective output is set to 1, while all other outputs remain 0. This is to prevent confusion over multiple digits being identified for the same input.

Method:

Recommended Approach: Rounding

Reasoning:

1. Precision Requirement:

- The goal of your circuit is to identify specific decimal digits of e . Since e has a non-terminating, non-repeating decimal expansion (approximately 2.7182818284), rounding is preferable to ensure that you accurately represent each digit.

2. Significant Digits:

- Since the digits after the decimal point are significant in many mathematical and engineering contexts, rounding helps provide a more accurate representation of those digits when needed.

3. Output Representation:

- For inputs representing decimal places, rounding ensures that if the digit of e falls exactly at a point where rounding decisions could be made (for example, at 2.718), the circuit outputs the nearest digit correctly.

Conclusion:

Digit Identifier Circuit for Euler's number e it is intended to provide precise identification of the specific decimal digits in dependence on the 4-bit binary input that codes decimal places ranging from 0 to 9. Every single eligible input directly relates to a certain output associated with the digit of an integer. Thereby reducing the level of obscurity to an insignificant level. The circuit also takes precautions to handle an error condition involving an invalid input – in this case, all of the outputs are zeroed. By implementing rounding for output representation, the circuit improves on the accuracy of detecting meaning digits of e . In conclusion, this project shows an adequate appreciation of digital design concepts and is satisfactory from the technical point of view in meeting digit identification objectives.